

Filter Transformation:-

Impedance scaling:

In the prototype design, the source and load resistance are unity (except for equal-ripple filters with even N , which has non unity load resistance). A source resistance of R_0 can be obtained by multiplying all the impedances of the prototype design by R_0 . Thus

$$L' = R_0 L$$

$$C' = C/R_0$$

$$R'_S = R_0$$

$$R'_L = R_0 R_L$$

where L , C , R_L are the component values for the original prototype.

Frequency scaling for low pass filters:



To change the cutoff frequency of the LPP to ω_c requires that we scale the frequency dependence of the filter by the factor $1/\omega_c$ which is accomplished by replacing ω by ω/ω_c .

$$\omega \leftarrow \omega/\omega_c$$

Then the new power loss ratio will be

$$P'_{LR}(\omega) = P_{LR}(\omega/\omega_c)$$

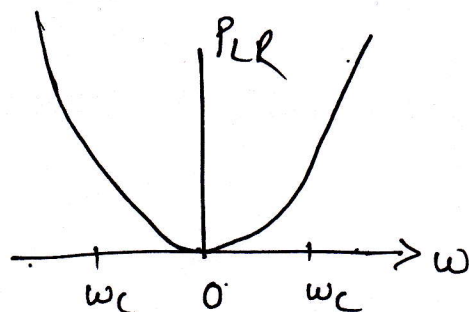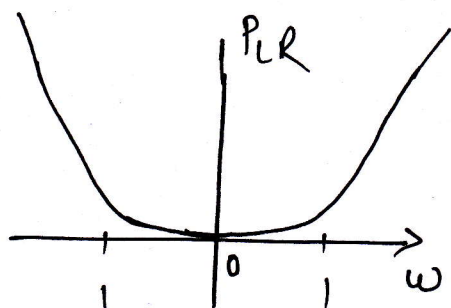where ω_c is the new cutoff frequency; cutoff occurs when $\omega/\omega_c = 1$ or, $\omega = \omega_c$. This transformation can be viewed as a stretching, or expansion, of the original pass band as illustrated in figure.



The new element values are determined by applying the substitution ($\omega \leftarrow \omega/\omega_c$) to the series reactance $j\omega L_k$ & shunt susceptance $j\omega C_k$ of prototype filter.

$$jX_k = j \frac{\omega}{\omega_c} L_k = j\omega L_k'$$

$$jB_k = j \frac{\omega}{\omega_c} C_k = j\omega C_k'$$

which shows,

$$L_k' = L_k / \omega_c$$

$$C_k' = \frac{C_k}{\omega_c}$$

when both impedance and frequency are scaled

$$L_k' = \frac{R_0 L_k}{\omega_c} \quad \& \quad C_k' = \frac{C_k}{R_0 \omega_c}$$

low pass to high pass transformation:

$\Rightarrow$ The frequency substitution $\omega \leftarrow -\omega_c/\omega$ can be used to convert a LPF to HPF. substitution maps $\omega=0$ to $\omega=\pm\infty$ & viceversa.

$$jX_k = -j \frac{\omega_c}{\omega} L_k = \frac{1}{j\omega C_k'}$$

$$jB_k = -j \frac{\omega_c}{\omega} C_k = \frac{1}{j\omega L_k'}$$

$$\therefore C_k' = \frac{1}{\omega_c L_k}$$

$$\& \quad L_k' = \frac{1}{\omega_c C_k}$$

impedance scaling can be included as

$$C_k' = \frac{1}{R_0 \omega_c L_k}$$

$$L_k' = \frac{R_0}{\omega_c C_k}$$

Low pass Filter Design:-

Insertion loss method

⇒ In insertion loss method a filter response is defined by its insertion loss lower or power loss ratio P_{LR}

$$P_{LR} = \frac{\text{Power available from source}}{\text{Power delivered to load}} = \frac{P_{inc}}{P_{load}}$$

$$P_{LR} = \frac{1}{1 - |\Gamma(\omega)|^2} \quad \text{--- (1)}$$

The quantity is reciprocal of $|S_{12}|^2$ if both load & source are matched.

The insertion loss (I_L) in dB is

$$I_L = 10 \log P_{LR}$$

From LPF Design we know $|\Gamma(\omega)|^2$ is even function of ω , therefore it can be expressed as a polynomial in ω^2 , thus we can write,

$$|\Gamma(\omega)|^2 = \frac{M(\omega^2)}{M(\omega^2) + N(\omega^2)} \quad \text{--- (2)}$$

This is sufficient condition to satisfy for physically realizable filter design using insertion loss method.

Maximally flat (Butterworth/Binomial filter)

Specified by

$$P_{LR} = 1 + K^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$

where, N is order of filter

ω_c = cutoff frequency

passband extends from $\omega = 0$ to $\omega = \omega_c$ at the edge power loss ratio is $1 + K^2$.

for $K = 1$

$$\omega \gg \omega_c \quad P_{LR} \approx K^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$

which shows that insertion loss increases at the rate of $20N$ dB/decade.

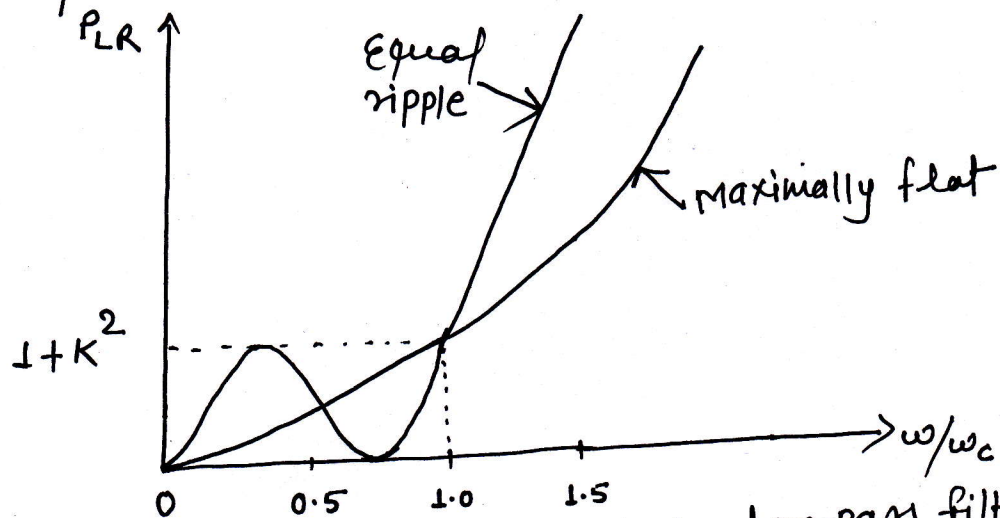


fig: Maximally flat and equal-ripple low-pass filter response (N=3)

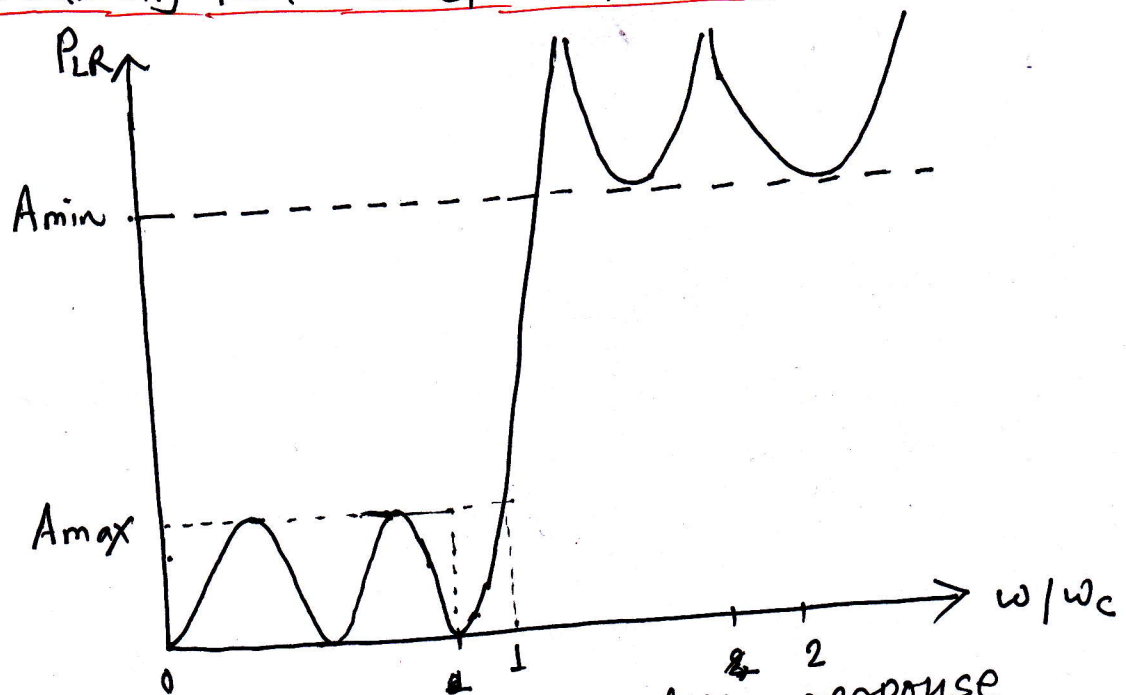


fig: Elliptic function low-pass filter response

For Equiripple (Chebyshev)


$$PLR = 1 + K^2 T_N^2(\omega/\omega_c)$$

$$T_N(x) = \pm 1 \text{ for } |x| \leq 1$$

$$T_N(x) \approx \frac{1}{2} (2x)^N \text{ for } \omega/\omega_c \gg 1$$

$$\therefore PLR = \frac{K^2}{4} \left(\frac{2\omega}{\omega_c} \right)^{2N}$$

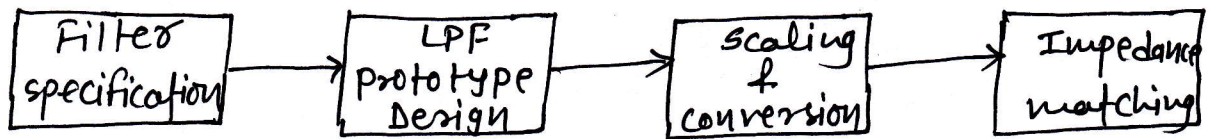Process flow block diagram by Insertion loss method:



Maximally flat LPF prototype:

we derive normalized value of L & C , assuming

$$R_s = 1 \Omega$$

$$\omega_c = 1 \text{ \& } N = 2$$

$$P_{LR} = H\omega^4 \text{ [} N = 2 \text{]}$$

Now,

$$Z_{in} = j\omega L + \frac{R(1-j\omega R_c)}{1+\omega^2 R^2 C^2}$$

Since $\Gamma = \frac{Z_{in}-1}{Z_{in}+1}$


$$P_{LR} = \frac{1}{1+|\Gamma|^2} = \frac{1}{1 - \left[\frac{(Z_{in}-1)}{(Z_{in}+1)} \right] \left[\frac{(Z_{in}^*-1)}{(Z_{in}^*+1)} \right]}$$

$$= \frac{|(Z_{in}+1)|^2}{2(Z_{in}+Z_{in}^*)}$$

Now,

$$Z_{in}+Z_{in}^* = \frac{2R}{1+\omega^2 R^2 C^2}$$

$$|Z_{in}+1|^2 = \left(\frac{R}{1+\omega^2 R^2 C^2} + 1 \right)^2 + \left(\omega L - \frac{\omega R^2}{1+\omega^2 R^2 C^2} \right)^2$$

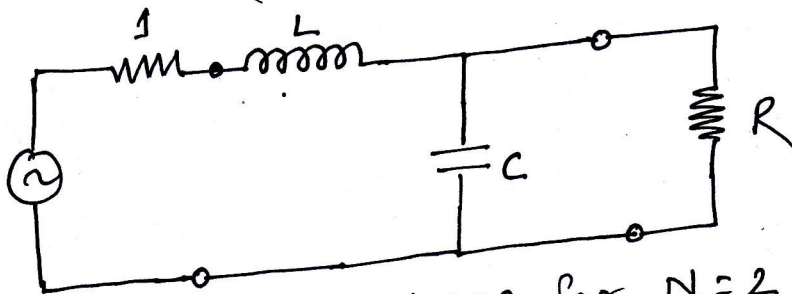

LPF prototype for $N=2$

$$P_{LR} = \frac{1+\omega^2 R^2 C^2}{4R} \left[\left(\frac{R}{1+\omega^2 R^2 C^2} + 1 \right)^2 + \left(\omega L - \frac{\omega R^2}{1+\omega^2 R^2 C^2} \right)^2 \right]$$

$$= \frac{1}{4R} (R^2 + 2R + 1 + R^2 \omega^2 C^2 + \omega^2 L^2 + \omega^4 L^2 C^2 R^2 - 2\omega^2 L C R^2)$$

$$= 1 + \frac{1}{4R} [(1-R)^2 + (R^2 C^2 + L^2 - 2LCR^2)\omega^2 + L^2 C^2 R^2 \omega^4]$$

Coefficient of ω^2 should vanish so
 $C^2 + L^2 - 2LC = 0$ or $(L - C)^2 = 0$


$$\therefore L = C$$

Coefficient of ω^4 must be unity, hence


$$\frac{1}{4} L^2 C^2 = \frac{1}{4} L^4 = 1$$

$$\therefore L = C = \sqrt{2}$$

gn general,

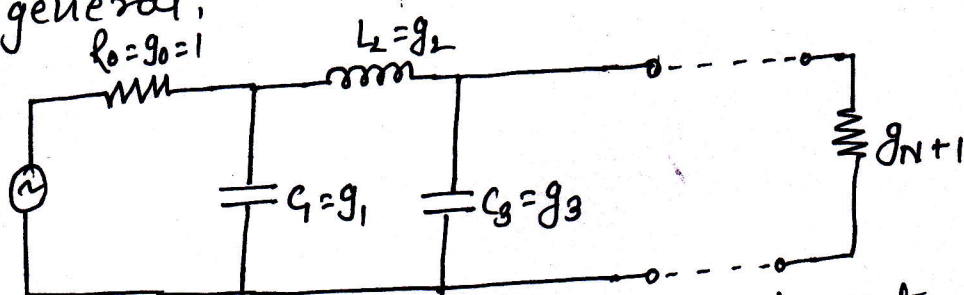

a) prototype with shunt element

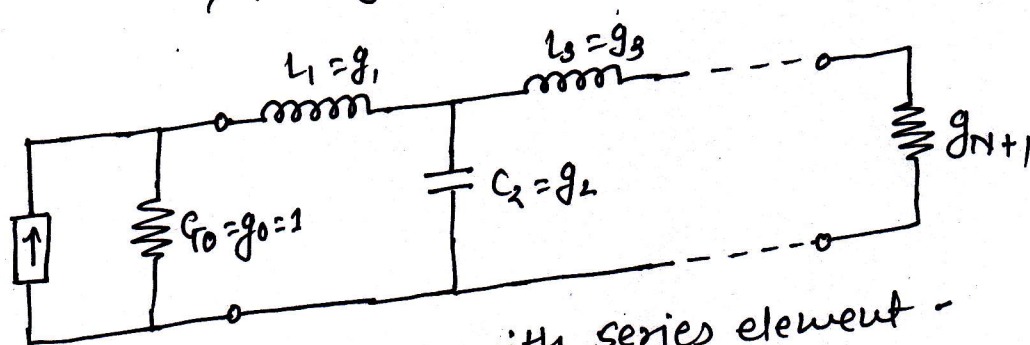

b) prototype with series element -

Equiripple LPF prototype:

$$P_{LR} = 1 + K^2 T_N^2(\omega)$$

$$T_N(0) = \begin{cases} 0 & \text{for } N \text{ odd} \\ 1 & \text{for } N \text{ even} \end{cases}$$

Microstrip implementation:-


⇒ we can implement LPF in microstrip or strip line by using alternating sections of very high & very low characteristic impedance lines.

These filters are also called stepped-impedance or high- z_0 , low- z_0 filters.

Advantages of using such filters are easier to design & take up less space than a similar low-pass filters using stubs.

Because of the approximations involved, however, their electrical performance is not as good, so the use of such filters is usually limited to applications where a sharp cutoff is not required.



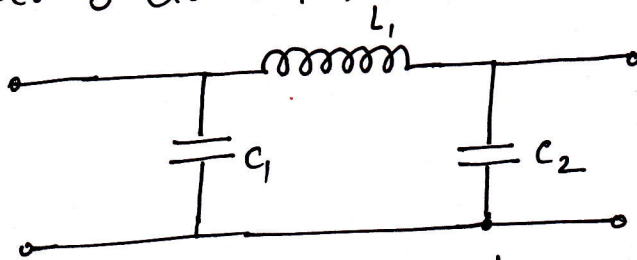
Consider 3-element filter with exact normalized values.




Replace C_1 with low z_0 transmission line

Replace L_2 with high z_0 transmission line

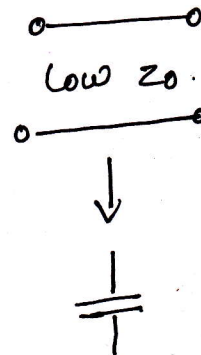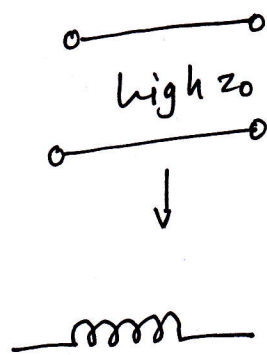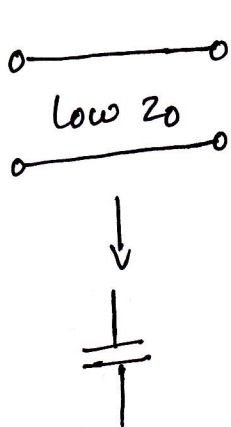Replace C_2 with low z_0 transmission line



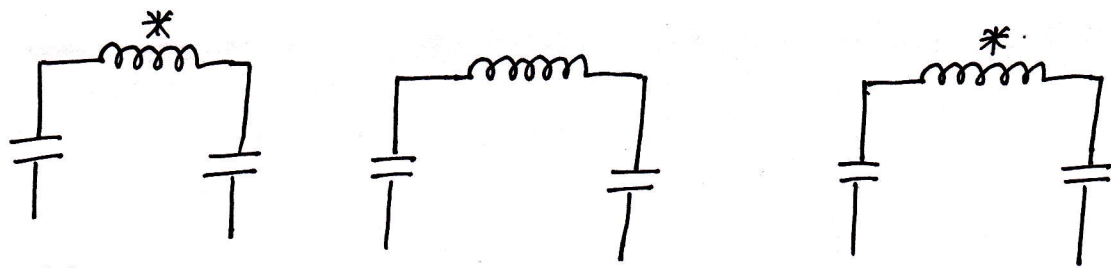⇒ each one of these sections can be replaced with the true model of transmission line.





* This inductance is ignorable.

$$\text{low } Z_0(C) \approx 20 \Omega$$


$$\text{high } Z_0(L) \approx 100 \Omega$$

$\Rightarrow$ if we can design with only these values for Z_0 we should then adjust the length.

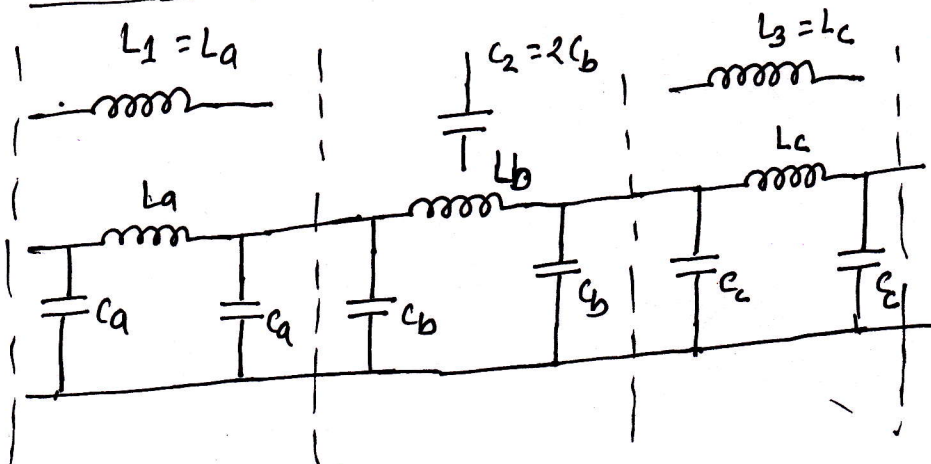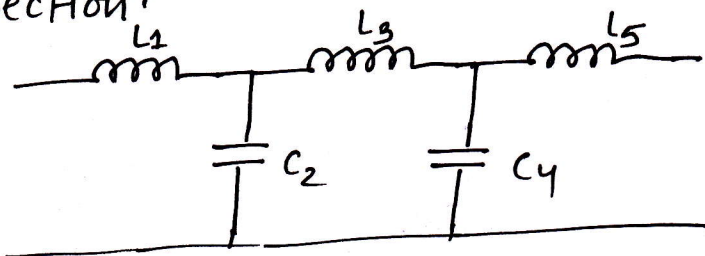
There will still be some capacitance in the inductor equivalent section.




This is approximately

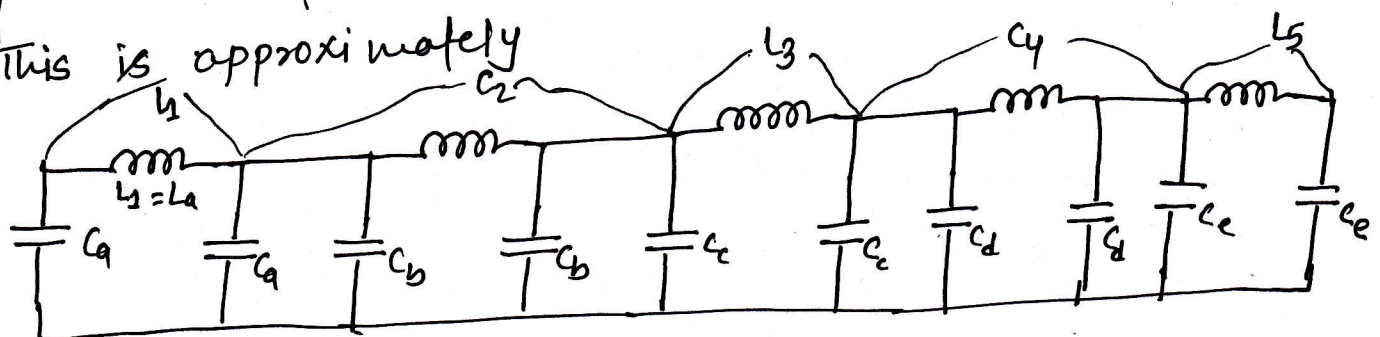


So,

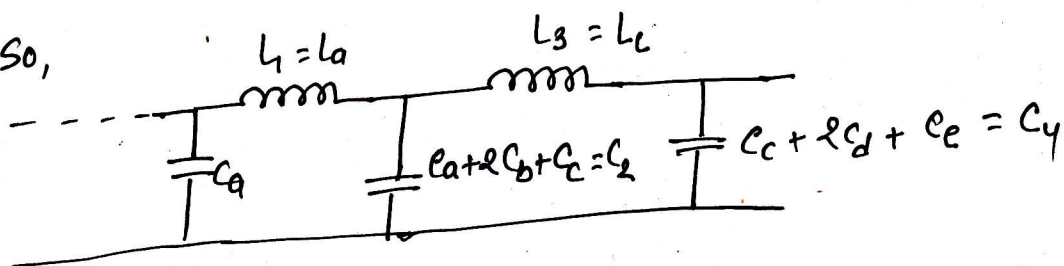

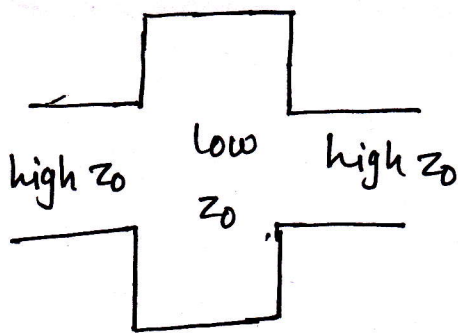


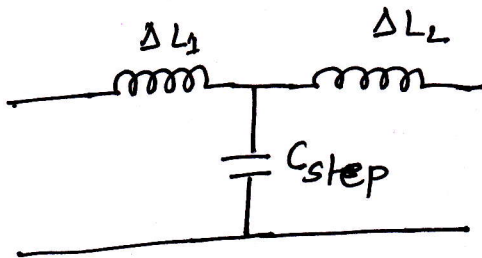we get junction transistor effects.
when we deal with microstrip.
discontinuities.



This equivalent ckt models a step.

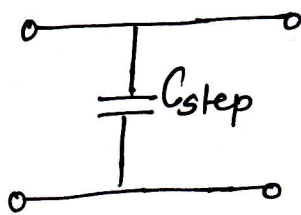→ since inductance values are small enough to ignore for our consideration.



we model this junction as a step.

⇒ This is different from the residual capacitance from the 'lumped' transmission line model. This is due to the geometry of the physical layout.

we have,

$$L_{eq} = \frac{Z_0 l}{v}$$

$$C_{eq} = \frac{l}{2 Z_0 v}$$

In terms of θ ,

$$L_{eq} = \frac{Z_0 l \beta}{\omega}$$

since $l = l_{eq}$ is at $\omega = 1$

$$L_{eq} = Z_0 \theta$$

$$\therefore \theta = \frac{L_{eq}}{Z_0} = \frac{l}{Z_0} \text{ --- (1)}$$

For capacitance,

$$C_{eq} = \frac{1}{2z_0 \omega} = \frac{1 \beta}{2 z_0 \omega}$$

$$2 C_{eq} = \frac{1 \beta}{z_0 \omega}$$

or, $2 C_{eq} = C$ is at $\omega = 1$

$$\Rightarrow \frac{\beta l}{z_0} = 2 C_{eq} = C$$

$$\therefore \theta = \beta l = C z_0 \text{ --- (2)}$$

At $\omega = \omega_c$, the electrical lengths because,

For inductor:

$$\theta = \beta l = \frac{L R_0}{z_0} = \frac{L R_0}{z_0} \text{ (inductor)}$$

For capacitor:

$$\theta = \beta l = \frac{C z_0}{R_0} \text{ (capacitor)}$$

where R_0 is the filter impedance & L & C are the normalized element values of the low-pass prototype.